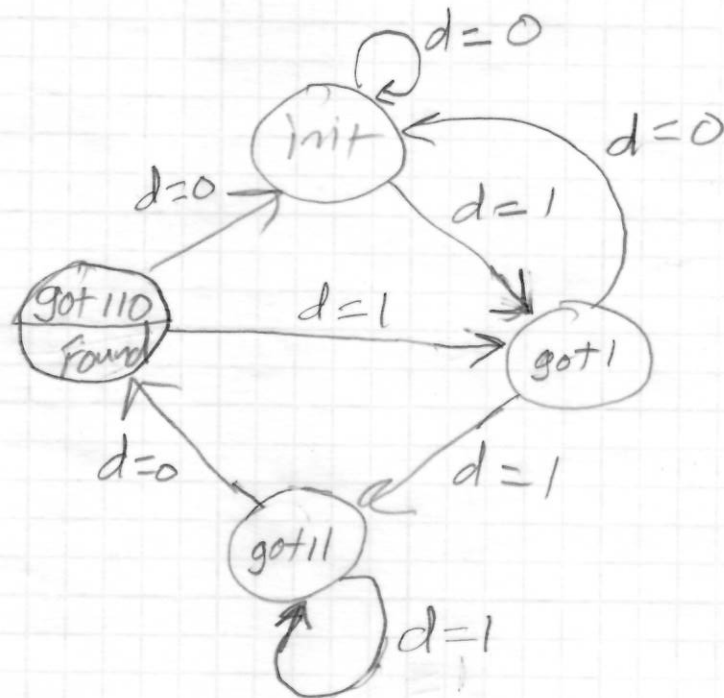


ECEN 340 Supplemental
 Example state machine to detect sequence,
 "110".

MOORE Machine State Graph:



MOORE Transition Table:

Inputs d	Current state	Next state	Outputs Found
0	INIT	INIT	0
1	INIT	got1	0
0	got1	INIT	0
1	got1	got11	0
0	got11	got110	0
1	got11	got11	0
0	got110	INIT	1
1	got110	got1	1

State Assignments:

INIT = 00
 got1 = 01
 got11 = 10
 got110 = 11

New transition table:

Current state		Inputs d	Next State		Outputs Found
Q_1	Q_0		N_1	N_0	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	0	1	1

Design Input Forming Logic (Next State)


$d \backslash Q_1 Q_0$	00	01	11	10
0	0	0	0	1
1	0	1	0	1

$$N_1 = Q_1' Q_0 d + Q_1 Q_0'$$


$d \backslash Q_1 Q_0$	00	01	11	10
0	0	0	0	1
1	1	0	1	0

$$N_0 = Q_1' Q_0' d + Q_1 Q_0 d + Q_1 Q_0' d'$$


Design output logic?

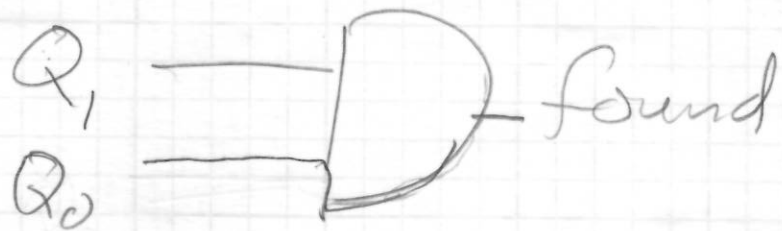

Draw circuit:

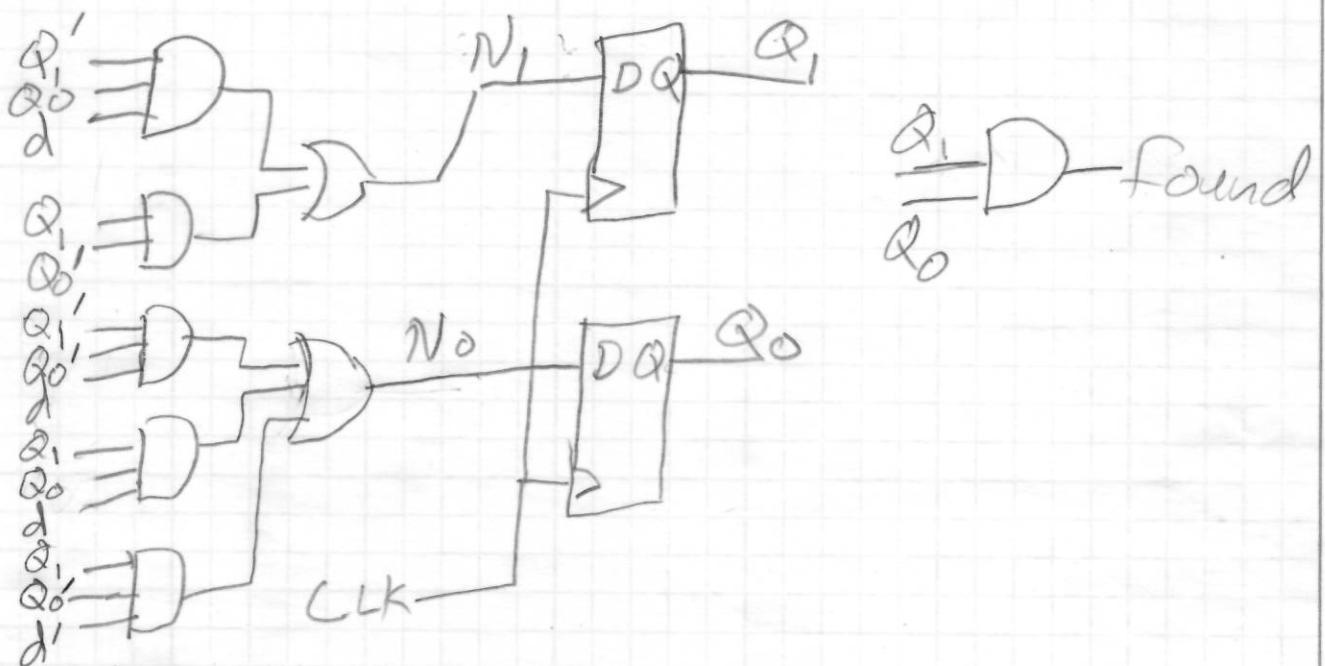

Timing Diagram for input = 10011011

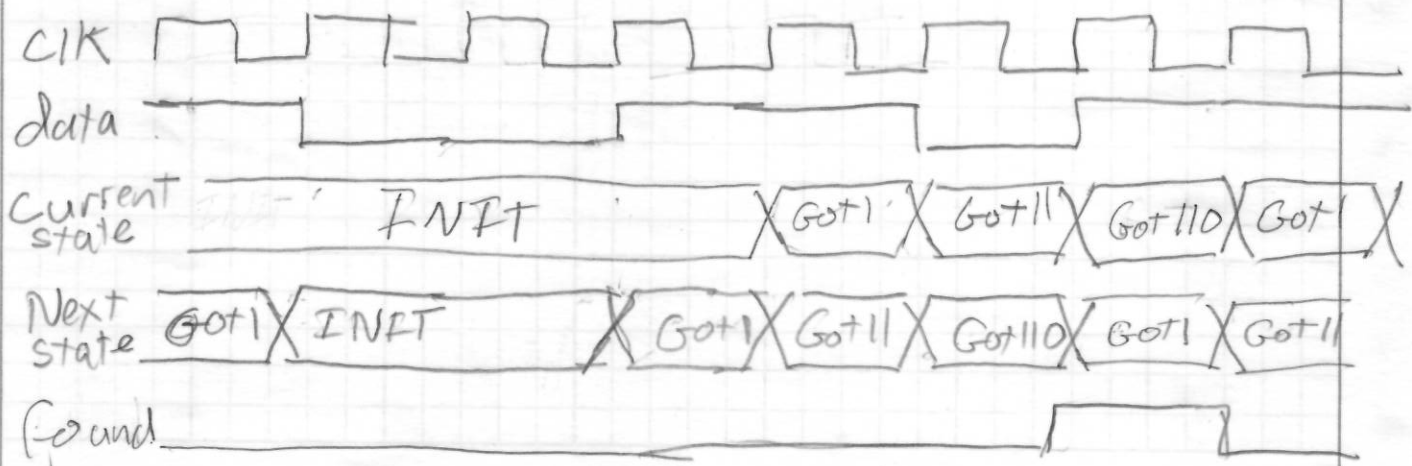

Design a Moaly State Graph
For the Same Application

